

# Stereo Audio Amplifier

Nathan Paternoster

Jena Macias

## **Description:**

We designed our stereo audio amplifier using the LM1877. The op-amp has feedback resistors  $R_f = 15k\Omega$  and input resistors  $R_i = 470\Omega$ . The left and right inputs are connected to the non-inverting terminals of the LM1877. The gain of each of the two non-inverting amps are therefore:

$$A_v = 1 + \frac{R_f}{R_i} = 1 + \frac{15k}{470} = +32.915$$

The op-amps are powered with a single voltage supply of +9V. The DC power supply has a *power-supply bypass capacitor* ( $C_B$ ) placed in parallel to remove any unwanted power-supply ripple voltage from appearing in the signal. A non-ideal DC voltage source will produce some small AC ripple that will introduce noise to the circuit. This capacitor will provide a path to ground for this AC ripple. The value of the capacitor will be  $0.1\mu F$ .

Two *coupling capacitors* ( $C_{i1}$  and  $C_{i2}$ ) are placed at the inputs. These will block the half-supply DC bias voltage (4.5V) from being fed back into the input (in this case our iPod). The values of these capacitors will be  $0.1\mu F$ . Likewise, two coupling capacitors ( $C_{o1}$  and  $C_{o2}$ ) will be placed at the output to prevent any DC voltage from appearing at the output. We are only interested in putting AC voltage to the output; the output coupling capacitors will block DC voltage from going to the speakers. The value of these capacitors will be large -  $470\mu F$ .

Normally an op-amp will contain some input offset voltage. This will be amplified at the output and produce noise. With very high gain, the DC offset voltages can cause the op-amp to exceed its rail voltages. There are two *DC stabilizing capacitors* ( $C_{DC1}$  and  $C_{DC2}$ ) placed at the inverting inputs of the op-amps. These will prevent the DC offsets from being amplified. With these caps the gain at DC will be unity and  $1 + \frac{R_f}{R_i}$  at all other frequencies. The value of these capacitors will be  $10\mu F$ .

*High-frequency compensation capacitors* ( $C_{HF1}$  and  $C_{HF2}$ ) are placed in parallel with the feedback resistor to remove high-frequency oscillations from occurring. These high-frequency oscillations occur


when parasitic capacitance at the op-amp's inputs combine with the feedback resistors. The HF compensations capacitors will provide a path for this capacitance so it won't travel through the feedback resistors. The values for these capacitors will be small – 22pF.

To further improve the quality of the output audio signal we included two “snubber” circuits – one at each op-amp's output. The snubber circuit consists of a path to ground that includes a resistor and a capacitor. Its purpose is to prevent any additional high-frequency oscillations (squeals) from appearing at the output. It basically acts as a low-pass filter at the output – removing higher frequencies from being put to the speakers. Both the resistor and capacitor will be small values – our resistors ( $R_{SN1}$  and  $R_{SN2}$ ) are  $10\Omega$  and the capacitors ( $C_{SN1}$  and  $C_{SN2}$ )  $0.1\mu\text{F}$ .



*Input impedance resistors* will be put at the input to set the input impedance of the op-amp to a non-infinite value. They will also ground the op-amp's input when no external input is connected so that the circuit's inputs won't be floating. They will be set to very large (but finite values). Our input impedance resistors ( $R_{M1}$  and  $R_{M2}$ ) will be  $1\text{M}\Omega$ .

Finally, our load will be a set of  $4\Omega$  speakers.

### Circuit:

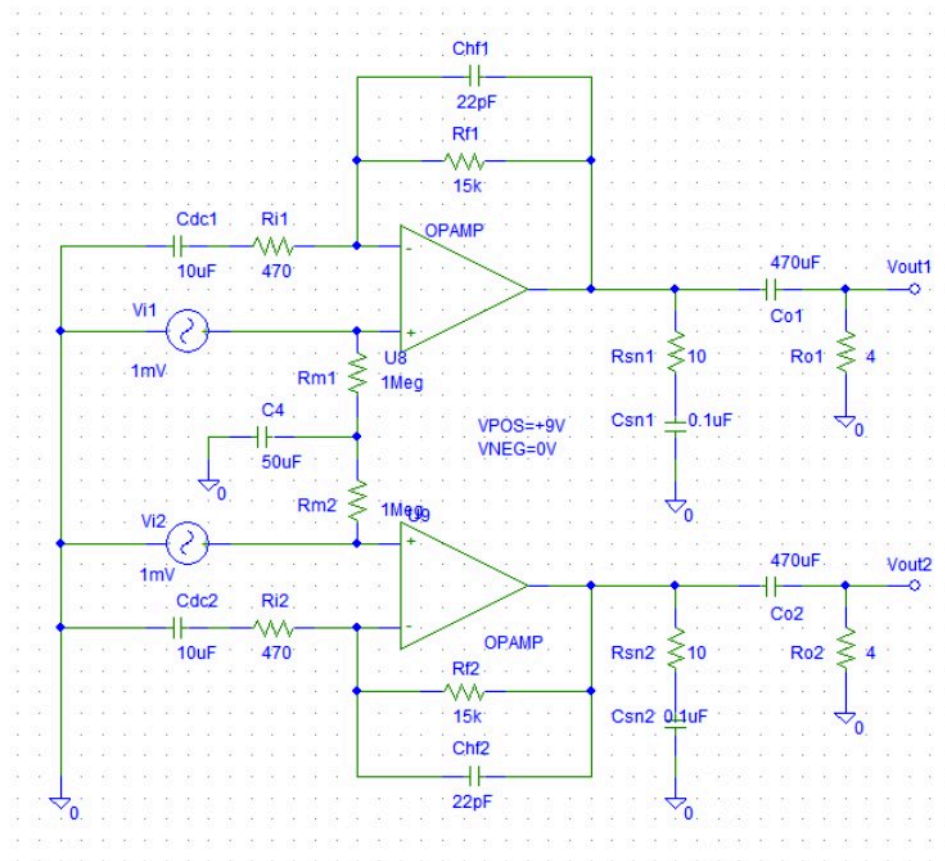

### Simulation:

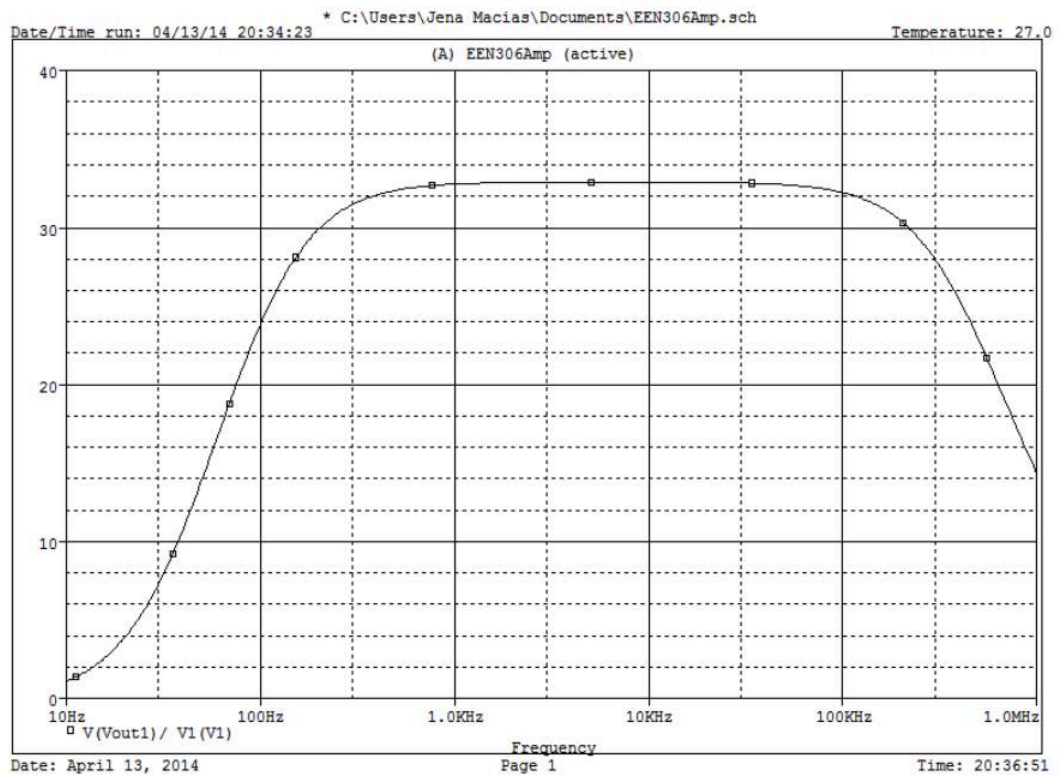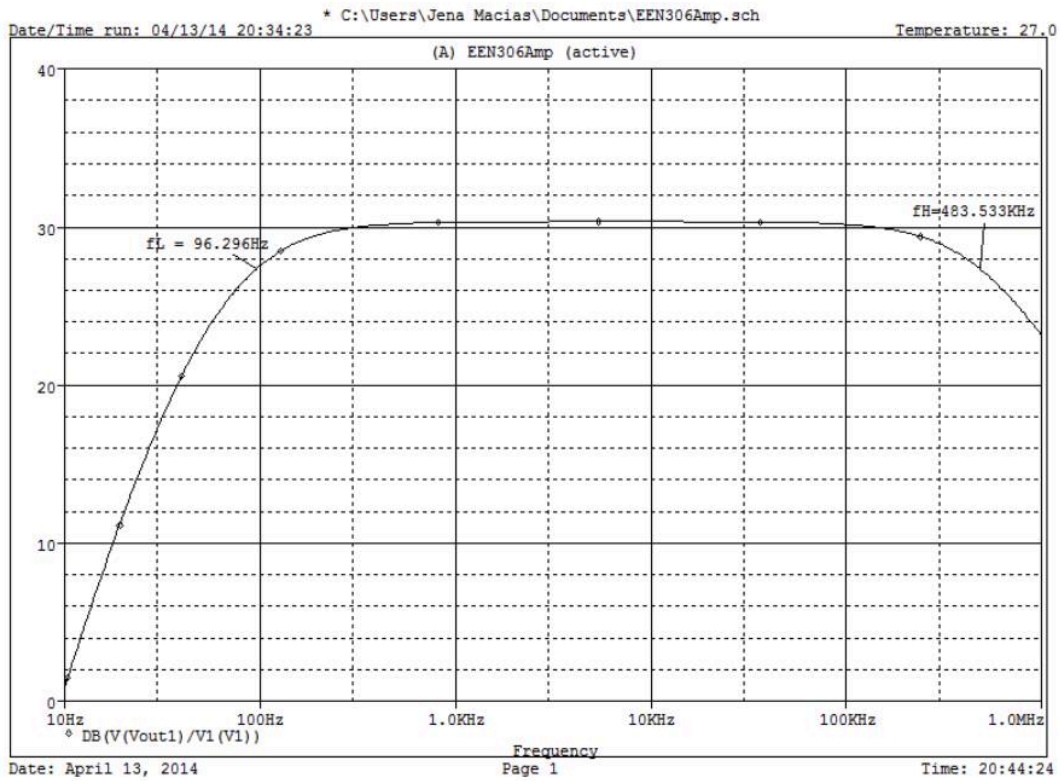

4/12/14

EEN306 – Final Project

**Pictures:**

